

Lab 04

Designing the Controller of the CPU

Category	Ryan Cruz ryan.cruz25@uga.edu	Zachary Davis zachdav@uga.edu
Pre-lab	50	50
In-lab Module & Testbench Design	50	50
In-lab Testbench Sim. & Analysis	50	50
In-lab FPGA Synthesis & Analysis	50	50
Lab Report Writing	50	50

February 8, 2018

Contents

1	Lab Purpose	3
2	Implementation Details	3
2.1	Part 1	3
2.2	Part 2	7
2.3	Part 3	7
3	Experimental Results	10
4	Significance	11
5	Comments/Suggestions	11

1 Lab Purpose

2 Implementation Details

2.1 Part 1

Prelab .

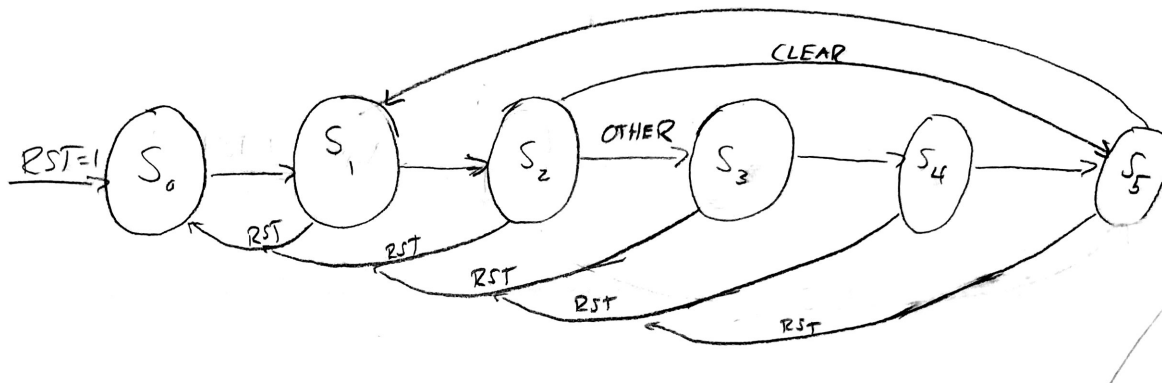


Figure 1: FSM for the controller of the CPU

Transition	LD_D	CL_D	LD_IR	CL_IR	LD_AC	CL_AC	ADD/SUB	R/W	MEM_EN	D/PC	LD_PC	PC_CNT	CL_PC
Any --> S0	0	1	0	1	0	1	0	0	0	0	0	0	1
S0 --> S1	0	0	0	0	0	0	0	0	1	1	0	0	0
S1 --> S2	0	0	1	0	0	0	0	0	0	1	0	1	0
S2 --> S5	0	0	0	0	0	1	0	0	0	1	0	0	0
S2 --> S3	0	0	0	0	0	0	0	0	1	1	0	0	0
S3 --> S4	1	0	0	0	0	0	0	0	0	1	0	0	0
S4 --> S5 Add	0	0	0	0	1	0	0	0	0	1	0	1	0
S4 --> S5 Sub	0	0	0	0	1	0	1	0	0	1	0	1	0
S4 --> S5 Store	0	0	0	0	0	0	0	1	1	0	0	1	0
S4 --> S5 BNZ (Z=1)	0	0	0	0	0	0	0	0	0	0	1	0	0
S4 --> S5 BNZ (Z=0)	0	0	0	0	0	0	0	0	0	0	0	1	0
S5 --> S1	0	0	0	0	0	0	0	0	0	1	0	0	0

Figure 2: Control Signals

$$\begin{aligned}
LD_D &= S_3 \\
CL_D &= RST \\
LD_IR &= S_1 \\
CL_IR &= RST \\
LD_AC &= S_4 \cdot (ADD + SUB) \\
CL_AC &= RST + S_2 \cdot CLEAR \\
ADDORSUB &= S_4 \cdot SUB \\
R/W &= S_4 \cdot STORE \\
D/PC &= [RST + S_4 \cdot (BNZ + STORE)]' \\
LD_PC &= S_4 \cdot BNZ \cdot ZERO \\
PC_CNT &= S_1 + S_4 \cdot [(ADD + SUB) + BNZ \cdot ZERO + STORE] \\
CL_PC &= RST \\
MEM_ENC &= S_1 + S_3 + S_4 \cdot STORE
\end{aligned}$$

Figure 3: Boolean Equations for figure 2. control signals

```

//control.v
`timescale 1s/1s

module control(CLK,CLR,RESET,S0,S1,S2,S3,S4,S5);

    input CLK;
    input CLR,RESET;
    output S0,S1,S2,S3,S4,S5;

    reg          S0,next_S0,
                S1,next_S1,
                S2,next_S2,
                S3,next_S3,
                S4,next_S4,
                S5,next_S5;

    reg          STATE0,next_STATE0,
                STATE1,next_STATE1,
                STATE2,next_STATE2,
                STATE3, next_STATE3,
                STATE4,next_STATE4,
                STATE5,next_STATE5;

```

```

always @(posedge CLK)
    begin
        STATE0 = next_STATE0;
        STATE1 = next_STATE1;
        STATE2 = next_STATE2;
        STATE3 = next_STATE3;
        STATE4 = next_STATE4;
        STATE5 = next_STATE5;
        S0 = next_S0;
        S1 = next_S1;
        S2 = next_S2;
        S3 = next_S3;
        S4 = next_S4;
        S5 = next_S5;
    end

always @ (CLR or RESET or STATE0 or STATE1 or STATE2 or STATE3
or STATE4 or STATE5)
    begin
        if ( RESET )
            next_STATE0=1;
        else
            next_STATE0=0;

        if ( ~RESET & STATE0 | ~RESET & STATE5 )
            next_STATE1=1;
        else
            next_STATE1=0;

        if ( ~RESET & STATE1 )
            next_STATE2=1;
        else
            next_STATE2=0;

        if ( ~RESET & ~CLR & STATE2 )
            next_STATE3=1;
        else
            next_STATE3=0;

        if ( ~RESET & STATE3 )
            next_STATE4=1;
        else
            next_STATE4=0;

        if ( ~RESET & CLR & STATE2 | ~RESET & STATE4 )
            next_STATE5=1;
    end

```

```

else
    next_STATE5=0;

if ( RESET )
    next_S0=1;
else
    next_S0=0;

if ( ~RESET & STATE0 | ~RESET & STATE5 )
    next_S1=1;
else
    next_S1=0;

if ( ~RESET & STATE1 )
    next_S2=1;
else
    next_S2=0;

if ( ~RESET & ~CLR & STATE2 )
    next_S3=1;
else
    next_S3=0;

if ( ~RESET & STATE3 )
    next_S4=1;
else
    next_S4=0;


if ( ~RESET & CLR & STATE2 | ~RESET & STATE4 )
    next_S5=1;
else
    next_S5=0;

end
endmodule

```

2.2 Part 2

2.3 Part 3

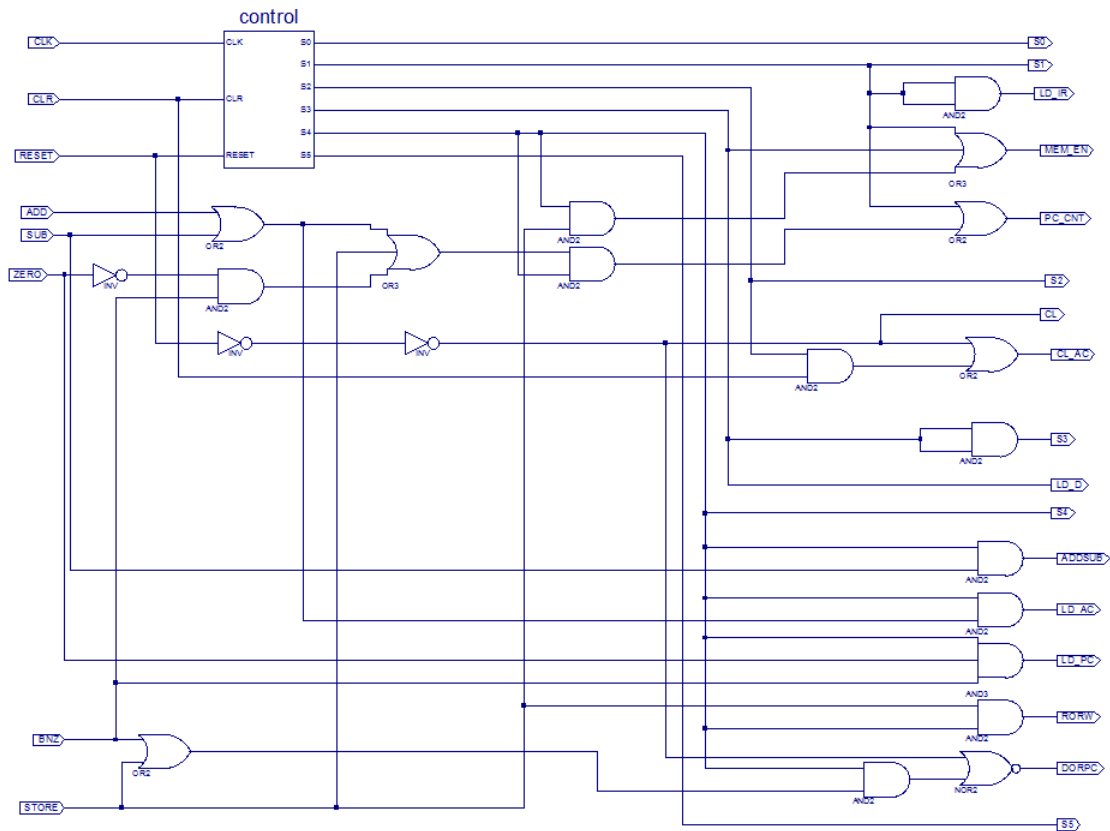

```
//controller_tb.v
`timescale 1ns/1ps

module controller_tbw_tb_0;

    reg ADD = 1'b0;
    reg BNZ = 1'b0;
    reg CLK = 1'b0;
    reg CLR = 1'b0;
    reg RESET = 1'b0;
    reg STORE = 1'b0;
    reg SUB = 1'b0;
    reg ZERO = 1'b0;

    wire ADDSUB;
    wire CL;
    wire CL_AC;
    wire DORPC;
```

```

wire LD_AC;
wire LD_D;
wire LD_IR;
wire LD_PC;
wire MEM_EN;
wire PC_CNT;
wire RORW;
wire S0;
wire S1;
wire S2;
wire S3;
wire S4;
wire S5;

initial // Clock process for CLK
begin
    forever
    begin
        CLK = 1'b0;
        #100;
        CLK = 1'b1;
        #100;
    end
end

controller_sch UUT(
    .ADD(ADD),
    .BNZ(BNZ),
    .CLK(CLK),
    .CLR(CLR),
    .RESET(RESET),
    .STORE(STORE),
    .SUB(SUB),
    .ZERO(ZERO),
    .ADDSUB(ADDSUB),
    .CL(CL),
    .CL_AC(CL_AC),
    .DORPC(DORPC),
    .LD_AC(LD_AC),
    .LD_D(LD_D),
    .LD_IR(LD_IR),
    .LD_PC(LD_PC),
    .MEM_EN(MEM_EN),
    .PC_CNT(PC_CNT),
    .RORW(RORW),
    .S0(S0),
    .S1(S1),

```



```

        .S2(S2),
        .S3(S3),
        .S4(S4),
        .S5(S5));

initial
begin
    // ----- Current Time: 85ns
    #85;
    RESET = 1'b1;
    // -----

    // ----- Current Time: 285ns
    #200;
    RESET = 1'b0;
    // -----

    // ----- Current Time: 485ns
    #200;
    CLR = 1'b1;
    // -----

    // ----- Current Time: 1085ns
    #600;
    ADD = 1'b1;
    CLR = 1'b0;
    // -----

    // ----- Current Time: 2085ns
    #1000;
    ADD = 1'b0;
    SUB = 1'b1;
    // -----

    // ----- Current Time: 3085ns
    #1000;
    STORE = 1'b1;
    SUB = 1'b0;
    // -----

    // ----- Current Time: 4085ns
    #1000;
    BNZ = 1'b1;
    STORE = 1'b0;
    // -----

    // ----- Current Time: 5085ns

```

```

#1000;
ZERO = 1'b1;
// -----

// ----- Current Time: 5885ns
#800;
ZERO = 1'b0;
// -----

// ----- Current Time: 6085ns
#200;
BNZ = 1'b0;
// -----

end
endmodule

```

3 Experimental Results

 


Figure 4:

[h]

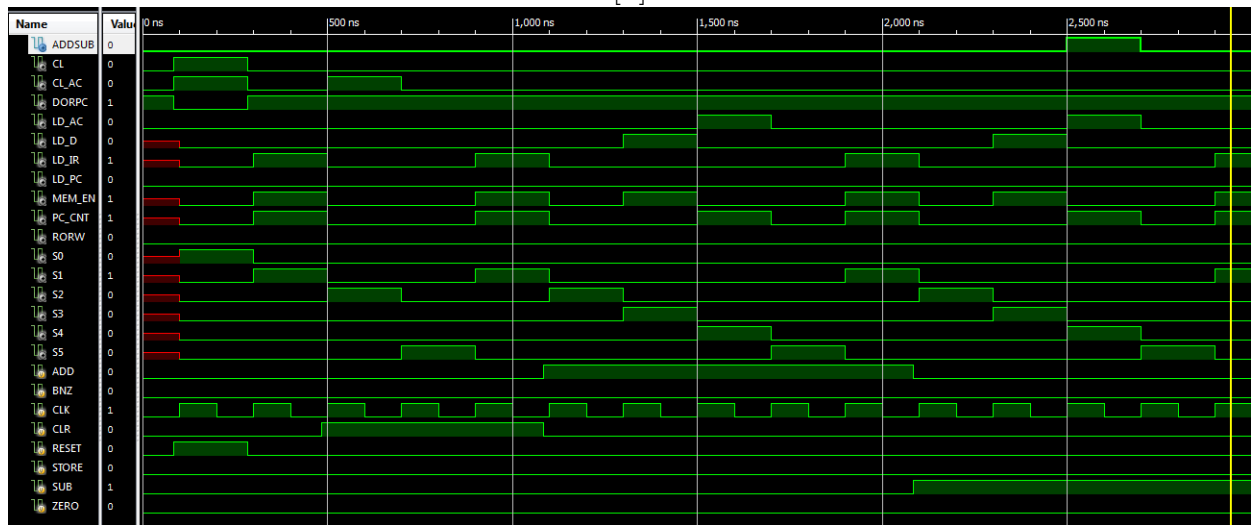


Figure 5:

4 Significance

5 Comments/Suggestions
