

Lab 04

Designing the Controller of the CPU

Category	Ryan Cruz ryan.cruz25@uga.edu	Zachary Davis zachdav@uga.edu
Pre-lab	50	50
In-lab Module & Testbench Design	50	50
In-lab Testbench Sim. & Analysis	50	50
In-lab FPGA Synthesis & Analysis	50	50
Lab Report Writing	50	50

February 8, 2018

Contents

1	Lab Purpose	3
2	Implementation Details	3
2.1	Part 1	3
2.2	Part 2	7
2.3	Part 3	8
3	Experimental Results	11
4	Significance	12
5	Comments/Suggestions	12

1 Lab Purpose

In this lab we design the controller for the CPU, covering all possible states and transitions layed out by the control signal table we completed for prelab (Figure 2.). Like always, all test cases will be tested with a test bench and corresponding waveforms, shown in the Expiremental Results section.

2 Implementation Details

2.1 Part 1

Prelab There were 3 parts to the prelab: Designing the FSM for the controller, the full control signal table, and the corresponding boolean equations for those signals.

 


Figure 1: FSM for the controller of the CPU. Created using information from the lecture slides

Transition	LD_D	CL_D	LD_IR	CL_IR	LD_AC	CL_AC	ADD/SUB	R/W	MEM_EN	D/PC	LD_PC	PC_CNT	CL_PC
Any --> S0	0	1	0	1	0	1	0	0	0	0	0	0	1
S0 --> S1	0	0	0	0	0	0	0	0	1	1	0	0	0
S1 --> S2	0	0	1	0	0	0	0	0	0	1	0	1	0
S2 --> S5	0	0	0	0	0	1	0	0	0	1	0	0	0
S2 --> S3	0	0	0	0	0	0	0	0	1	1	0	0	0
S3 --> S4	1	0	0	0	0	0	0	0	0	1	0	0	0
S4 --> S5 Add	0	0	0	0	1	0	0	0	0	1	0	1	0
S4 --> S5 Sub	0	0	0	0	1	0	1	0	0	1	0	1	0
S4 --> S5 Store	0	0	0	0	0	0	0	1	1	0	0	1	0
S4 --> S5 BNZ (Z=1)	0	0	0	0	0	0	0	0	0	0	1	0	0
S4 --> S5 BNZ (Z=0)	0	0	0	0	0	0	0	0	0	0	0	1	0
S5 --> S1	0	0	0	0	0	0	0	0	0	1	0	0	0

Figure 2: Control Signals. Filled in using states from the lecture slides using one-hot encoding, left any not-on state 0.

$$\begin{aligned}
LD_D &= S_3 \\
CL_D &= RST \\
LD_IR &= S_1 \\
CL_IR &= RST \\
LD_AC &= S_4 \cdot (ADD + SUB) \\
CL_AC &= RST + S_2 \cdot CLEAR \\
ADDORSUB &= S_4 \cdot SUB \\
R/W &= S_4 \cdot STORE \\
D/PC &= [RST + S_4 \cdot (BNZ + STORE)]' \\
LD_PC &= S_4 \cdot BNZ \cdot ZERO \\
PC_CNT &= S_1 + S_4 \cdot [(ADD + SUB) + BNZ \cdot ZERO' + STORE] \\
CL_PC &= RST \\
MEM_ENC &= S_1 + S_2 + S_4 \cdot STORE
\end{aligned}$$

Figure 3: Boolean Equations for figure 2. control signals

```

//control.v
`timescale 1s/1s

module control(CLK,CLR,RESET,S0,S1,S2,S3,S4,S5);

    input CLK;
    input CLR,RESET;
    output S0,S1,S2,S3,S4,S5;

    reg          S0,next_S0,
                S1,next_S1,
                S2,next_S2,
                S3,next_S3,
                S4,next_S4,
                S5,next_S5;

    reg          STATE0,next_STATE0,
                STATE1,next_STATE1,
                STATE2,next_STATE2,
                STATE3, next_STATE3,
                STATE4,next_STATE4,
                STATE5,next_STATE5;

    always @(posedge CLK)
        begin
            STATE0 = next_STATE0;
            STATE1 = next_STATE1;
            STATE2 = next_STATE2;
            STATE3 = next_STATE3;
            STATE4 = next_STATE4;
            STATE5 = next_STATE5;
            S0 = next_S0;
            S1 = next_S1;
            S2 = next_S2;
            S3 = next_S3;
            S4 = next_S4;
            S5 = next_S5;
        end

    always @ (CLR or RESET or STATE0 or STATE1 or STATE2 or STATE3
              or STATE4 or STATE5)
        begin
            if ( RESET )
                next_STATE0=1;
            else
                next_STATE0=0;
        end

```

```

if ( ~RESET & STATE0 | ~RESET & STATE5 )
    next_STATE1=1;
else
    next_STATE1=0;

if ( ~RESET & STATE1 )
    next_STATE2=1;
else
    next_STATE2=0;

if ( ~RESET & ~CLR & STATE2 )
    next_STATE3=1;
else
    next_STATE3=0;

if ( ~RESET & STATE3 )
    next_STATE4=1;
else
    next_STATE4=0;

if ( ~RESET & CLR & STATE2 | ~RESET & STATE4 )
    next_STATE5=1;
else
    next_STATE5=0;

if ( RESET )
    next_S0=1;
else
    next_S0=0;

if ( ~RESET & STATE0 | ~RESET & STATE5 )
    next_S1=1;
else
    next_S1=0;

if ( ~RESET & STATE1 )
    next_S2=1;
else
    next_S2=0;

if ( ~RESET & ~CLR & STATE2 )
    next_S3=1;
else
    next_S3=0;

if ( ~RESET & STATE3 )
    next_S4=1;

```

```

        else
            next_S4=0;

        if ( ~RESET & CLR & STATE2 | ~RESET & STATE4 )
            next_S5=1;
        else
            next_S5=0;
    end
endmodule

```

Runs through every case assigning states for each possible transition using simple if/else statements. Named each state and transition using variables in verilog.

2.2 Part 2

1-Hot Encoding For this part of the lab we needed to determine how we were going to encode the instruction register and the lab report recommended 1-hot encoding. We have five instructions to encode and an eight bit instruction register so rather than count up by ones we count up in powers of two. This reduces the number of labels sufficiently, but we only need five and with counting by powers of two there are eight combinations. This is far easier to construct in a schematic and far more human readable.

Instruction	Encoded Value (Decimal)	Encoded Value (Binary)
ADD	1	00000001
SUB	2	00000010
CLR	4	00000100
BNZ	8	00001000
STR	16	00010000

2.3 Part 3

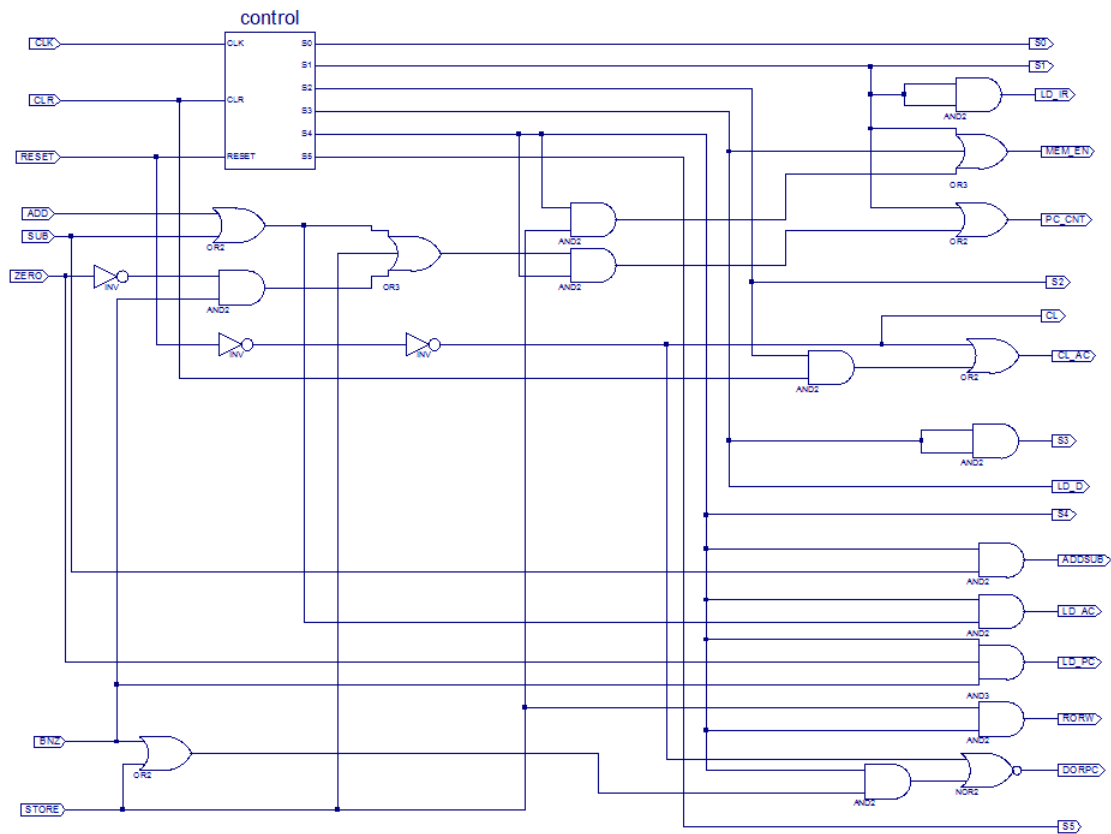


Figure 4: Schematic for the controller using a symbol for the control module we created in part 1.

```
//controller_tb.v
`timescale 1ns/1ps

module controller_tbw_tb_0;

    reg ADD = 1'b0;
    reg BNZ = 1'b0;
    reg CLK = 1'b0;
    reg CLR = 1'b0;
    reg RESET = 1'b0;
    reg STORE = 1'b0;
    reg SUB = 1'b0;
    reg ZERO = 1'b0;

    wire ADDSUB;
    wire CL;
    wire CL_AC;
```



```

wire DORPC;
wire LD_AC;
wire LD_D;
wire LD_IR;
wire LD_PC;
wire MEM_EN;
wire PC_CNT;
wire RORW;
wire S0;
wire S1;
wire S2;
wire S3;
wire S4;
wire S5;

initial // Clock process for CLK
begin
    forever
    begin
        CLK = 1'b0;
        #100;
        CLK = 1'b1;
        #100;
    end
end

controller_sch UUT(
    .ADD(ADD),
    .BNZ(BNZ),
    .CLK(CLK),
    .CLR(CLR),
    .RESET(RESET),
    .STORE(STORE),
    .SUB(SUB),
    .ZERO(ZERO),
    .ADDSUB(ADDSUB),
    .CL(CL),
    .CL_AC(CL_AC),
    .DORPC(DORPC),
    .LD_AC(LD_AC),
    .LD_D(LD_D),
    .LD_IR(LD_IR),
    .LD_PC(LD_PC),
    .MEM_EN(MEM_EN),
    .PC_CNT(PC_CNT),
    .RORW(RORW),
    .S0(S0),

```

```

        .S1(S1),
        .S2(S2),
        .S3(S3),
        .S4(S4),
        .S5(S5));

initial
begin
    // ----- Current Time: 85ns
    #85;
    RESET = 1'b1;
    // -----

    // ----- Current Time: 285ns
    #200;
    RESET = 1'b0;
    // -----

    // ----- Current Time: 485ns
    #200;
    CLR = 1'b1;
    // -----

    // ----- Current Time: 1085ns
    #600;
    ADD = 1'b1;
    CLR = 1'b0;
    // -----

    // ----- Current Time: 2085ns
    #1000;
    ADD = 1'b0;
    SUB = 1'b1;
    // -----

    // ----- Current Time: 3085ns
    #1000;
    STORE = 1'b1;
    SUB = 1'b0;
    // -----

    // ----- Current Time: 4085ns
    #1000;
    BNZ = 1'b1;
    STORE = 1'b0;
    // -----

```

```

// ----- Current Time: 5085ns
#1000;
ZERO = 1'b1;
// -----

// ----- Current Time: 5885ns
#800;
ZERO = 1'b0;
// -----

// ----- Current Time: 6085ns
#200;
BNZ = 1'b0;
// -----

end

endmodule

```

3 Experimental Results

 


Figure 5: Test bench for the control module. The uniform cascading waves show the simple transitions from 0-5, and at the bottom you can see that when clear is active, S5 occurs, and when reset is active, S0 occurs.

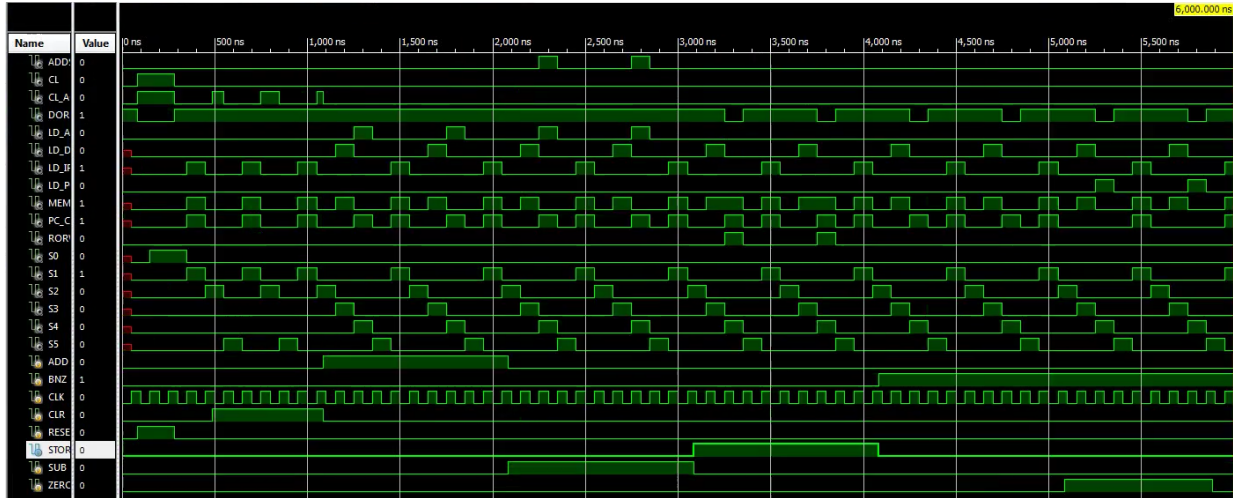


Figure 6: Test bench for the controller schematic. Cycles clock every 100 ns and changes all states to cover all cases. The inputs line the bottom, and the outputs exist on top. The cascading S0-S5 waves that look similar to the first test bench are exactly that, more direct state transitions. Then you can see things like CL_A activating when CLR and S2 are 1, CL on RESET, RORW on STORE and S4, and the rest of the things that occur in the table.

4 Significance

Another piece of the full CPU puzzle, the controller allows us to take in any of the control signals and provide the correct instructions to the CPU. With this controller completed, we can move on to connect this portion to the datapath to complete and assemble the toy processor, which will be able to run a given program.

5 Comments/Suggestions
