

Lab 07

Toy Processor with Memory on the Basys2 Board

Category	Ryan Cruz ryan.cruz25@uga.edu	Zachary Davis zachdav@uga.edu
Pre-lab	50	50
In-lab Module & Testbench Design	50	50
In-lab Testbench Sim. & Analysis	50	50
In-lab FPGA Synthesis & Analysis	50	50
Lab Report Writing	50	50

March 28, 2018

Contents

1	Lab Purpose	3
2	Implementation Details	3
2.1	Part 1 - Clock and Bypass Circuits	3
2.2	Part 2 - Programming the Basys2 Board	7
3	Experimental Results	10
4	Significance	11
5	Comments/Suggestions	11

1 Lab Purpose

With the design of the toy processor complete, we can now implement it physically. With some tweaks to make it compatible, we can put it on the Basys2 board and load some simple programs onto it.

2 Implementation Details

2.1 Part 1 - Clock and Bypass Circuits

Clock

The clock for the processor, when implemented on the board, will be provided by the board. This clock is too fast for human reading, so we will generate a push button clock and step through each operation.

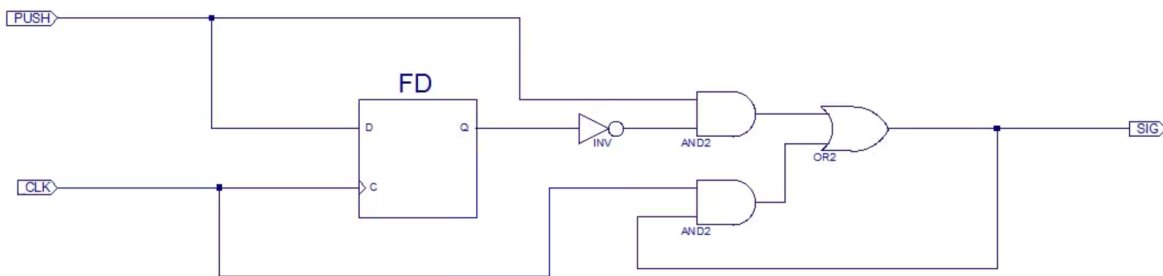


Figure 1: Design of the clock signal created in Xilinx. (Designed on paper but just turned in a print out of this for prelab)

```
//Clock Testbench
'timescale 1ns/1ps

module clk_signal_tb;

    reg CLK = 1'b0;
    reg PUSH = 1'b0;

    wire SIG;

    initial // Clock process for CLK
        begin
            forever
                begin
                    CLK = 1'b0;
                    #100;
                end
            end
        end
```



```

`timescale 1ns/1ps

module BypassClk_tb;

    reg CLK = 1'b0;
    reg OVERFLOW = 1'b0;
    reg PUSH = 1'b0;
    reg RESET = 1'b0;

    wire Signalout;

    initial // Clock process for CLK
        begin
            forever
            begin
                CLK = 1'b0;
                #50;
                CLK = 1'b1;
                #50;
            end
        end

    BypassClk UUT (
        .CLK(CLK),
        .OVERFLOW(OVERFLOW),
        .PUSH(PUSH),
        .RESET(RESET),
        .Signalout(Signalout));

    initial
        begin
            // ----- Current Time: 140ns
            #140;
            RESET = 1'b1;
            // -----

            // ----- Current Time: 340ns
            #200;
            RESET = 1'b0;
            // -----

            // ----- Current Time: 440ns
            #100;
            PUSH = 1'b1;
            // -----

            // ----- Current Time: 640ns

```

```

#200;
PUSH = 1'b0;
// -----

// ----- Current Time: 740ns
#100;
PUSH = 1'b1;
// -----

// ----- Current Time: 840ns
#100;
PUSH = 1'b0;
// -----

// ----- Current Time: 940ns
#100;
OVERFLOW = 1'b1;
// -----

// ----- Current Time: 1040ns
#100;
OVERFLOW = 1'b0;
// -----

// ----- Current Time: 2140ns
#200;
PUSH = 1'b1;
// -----

// ----- Current Time: 2340ns
#200;
PUSH = 1'b0;
#100;
PUSH = 1'b1;
#100;
PUSH = 1'b0;
// -----

end

endmodule

```

To make the processor compatible with the board and for it to be testable, we must program the seven segment display, similar to how we have done in previous labs. It will display the instructions, as well as the accumulator.



With the board ready for programs, we can now enter machinecode into ROM and actually see its output on the seven segment display. We will design two programs, with the 2nd testing all of the capabilities of our ToyProcessor.

The first program that we will load onto the board simply sums the numbers from 1-9 using the ADD instruction and then stores that sum. This program is not self-modifying, does not loop, and is linear – it ends after the first run.

First Serial Addition Program

Address	Instruction	Description
0	100	CLR
1	1	ADD
2	1	1
3	1	ADD
4	10	2
5	1	ADD
6	11	3
7	1	ADD
8	100	4
9	1	ADD
10	101	5
11	1	ADD
12	110	6
13	1	ADD
14	111	7
15	1	ADD
16	1000	8
17	1	ADD
18	1001	9
19	10000	STORE
20	45	45

Second Serial Addition Program

Address	Instruction	Description
0	100	CLR
1	1	ADD
2	1010	10
3	10	SUB
4	1	1
5	10000	STORE
6	10	2
7	1000	BNZ
8	10010	18
9	1	ADD
10	0	0
11	10000	STORE
12	1010	10
13	10000	STORE
14	1100100	100
15	100	CLR
16	1000	BNZ
17	1	1

3 Experimental Results

4 Significance

With memory added, we have much more flexibility with what we can input to the Toy Processor. Also, it is

5 Comments/Suggestions

N.A.